

# LM3478,LM3488

*Application Note 1204 LM3478/LM3488 Evaluation Board*



Literature Number: SNVA042A

# LM3478/LM3488 Evaluation Board

National Semiconductor  
Application Note 1204  
Chance Dunlap  
July 2002



## Introduction


The LM3478 and LM3488 are current mode, low side N channel FET controllers. They can be utilized in numerous configurations including a Boost, Flyback or SEPIC (Single Ended Primary Inductor Converter). This evaluation board demonstrates the flexibility of the LM3478 in a boost topology. The operating conditions for the evaluation board are listed below:

$$4.5V \leq V_{IN} \leq 5.5V$$

$$V_{OUT} = 12V$$

$$0A \leq I_{OUT} \leq 1.5A$$

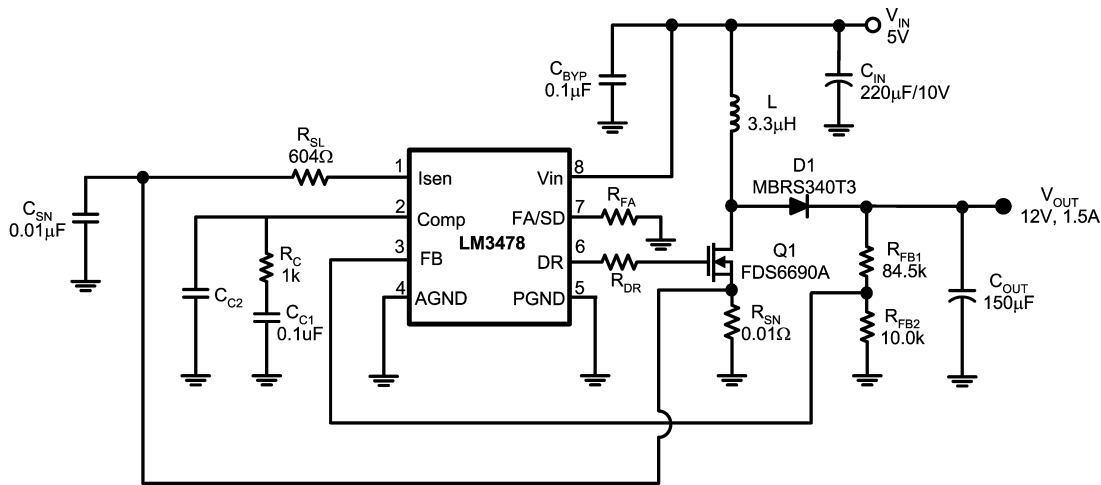The circuit and bill of materials for this design are given below:



20023502


FIGURE 1. Circuit Diagram

TABLE 1. Bill of Materials

Component	Value	Model Number
U1		LM3478
L1	3.3μH	DO3316P-332 (Coilcraft)
Q1	30V/11A	FDS6690A (Fairchild)
D1	100V/3A	MBRS340T3 (Motorola)
C <sub>IN</sub>	Tantalum, 220μF/10V	595D227X9010R2 (Sprague)
C <sub>OUT</sub>	Tantalum, 150μF/16V	595D157X9016R2 (Sprague)
C <sub>OUT1</sub>	No Connect	
C <sub>C1</sub>	0.1μF/25V	VJ0805Y104KXXA (Vitramon)
C <sub>C2</sub>	No Connect	
C <sub>BYN</sub>	0.1μF/25V	VJ0805Y104KXXA (Vitramon)
C <sub>SEN</sub>	0.01μF/25V	VJ0805Y103KXXA (Vitramon)
R <sub>FB1</sub>	84.5kΩ	CRCW08058452 (Vitramon)
R <sub>FB2</sub>	10kΩ	CRCW08051002 (Vitramon)
R <sub>C</sub>	1kΩ	CRCW08051001 (Vitramon)
R <sub>SEN</sub>	0.010Ω	(Dale, 1%, 1W, R01F, 2512)
R <sub>DR</sub>	0Ω	CRCW0805600R0 (Vitramon)
R <sub>S1</sub>	604Ω	CRCW08056040 (Vitramon)
R <sub>FA</sub>	40.2kΩ	CRCW08054022 (Vitramon)
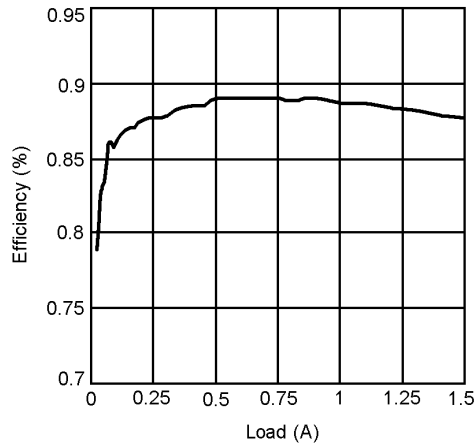
## Performance


Benchmark data has been taken from the evaluation board using the LM3478. *Figure 2* shows an efficiency measurement taken at the maximum load of 1.5A with  $V_{in}$  at 5V.



20023503

**FIGURE 2. Efficiency vs Load**

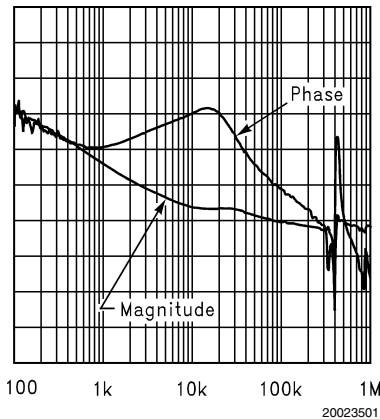The open loop frequency response was also measured using the evaluation board as specified in the bill of materials. The bode plot can be seen below in *Figure 3*.



20023501

**FIGURE 3. Frequency Response**

The advantage of the evaluation board is the ability to examine performance tradeoffs through substitution of parts. By careful selection of the components used, it is possible to optimize the application circuit for a given parameter. For instance, the FET footprint has been designed to accommodate either a SO-8 or SOT23-6 package. The selection of FET would then be determined by the design constraints. An example would be that a lower system cost could be obtained by selection of a FET with a higher  $R_{DS(ON)}$ , although performance would be sacrificed through reduced efficiency.

## Current Limit

The purpose of the  $R_{SL}$  resistor is to provide flexibility in the selection of the slope compensation needed for the required application. The amount of slope compensation directly determines the minimum inductance required for stability. (Please see the LM3478 or LM3488 datasheet for adjustment of slope compensation). In addition to slope compensation  $R_{SL}$  also provides assistance in the adjustment of current limit. Current limit is usually solely determined by the value of the sense resistor  $R_{sn}$ . But in the LM3478 and LM3488 an increase in  $R_{SL}$  causes the current limit to decrease by a slight amount. This can be advantageous in several situations. Common sense resistor values are typically separated by large intervals, making the task of accurately setting the current limit in any application difficult. As a result current limit is often ignored during the design phase, which can cause the application to suffer. An excessively high current limit can result in startup problems if the cycle-by-cycle current limit does not engage, limiting the effect of the soft start feature. Or worse, current limit could be set to low causing the output voltage to drop at the maximum load. This is where the  $R_{SL}$  resistor can be used to avoid these issues. By selecting a common value sense resistor, current limit can be accurately set by calculating the  $R_{SL}$  size needed. This eliminates the need to choose custom sense resistors that can be cost prohibitive and cause production issues because of the difficulty in obtaining an adequate supply. For a complete discussion on how to calculate the  $R_{SL}$  value needed, refer to the current limit section in the LM3478 or LM3488 datasheet.

## Layout Fundamentals

Good layout for DC-DC converters can be implemented by following a few simple design guidelines:

1. Place the power components (catch diode, inductor, and filter capacitors) close together. Make the traces between them as short and wide as possible.
2. Use wide traces between the power components and for power connections to the DC-DC converter circuit.
3. Connect the ground pins of the input and output filter capacitors and catch diode as close as possible using generous component-side copper fill as a pseudo-ground plane. Then, connect this to the ground plane through several vias.
4. Arrange the power components so that the switching loops curl in the same direction.
5. Separate noise sensitive traces, such as the voltage feedback path, from noisy traces associated with the power components.
6. Ensure a good low-impedance ground for the converter IC.
7. Place the supporting components for the converter IC, such as compensation and frequency selection components as close to the converter IC as possible, but away from noisy traces and the power components. Make their connections to the converter IC and its pseudo-ground plane as short as possible.
8. Place noise sensitive circuitry such as radio or modem blocks away from the DC-DC converter.

# Layout Fundamentals (Continued)

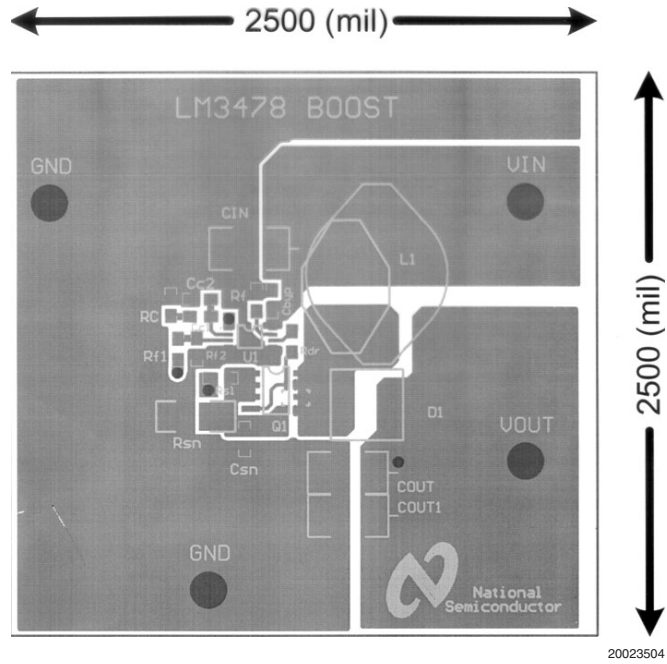


FIGURE 4. Front Side

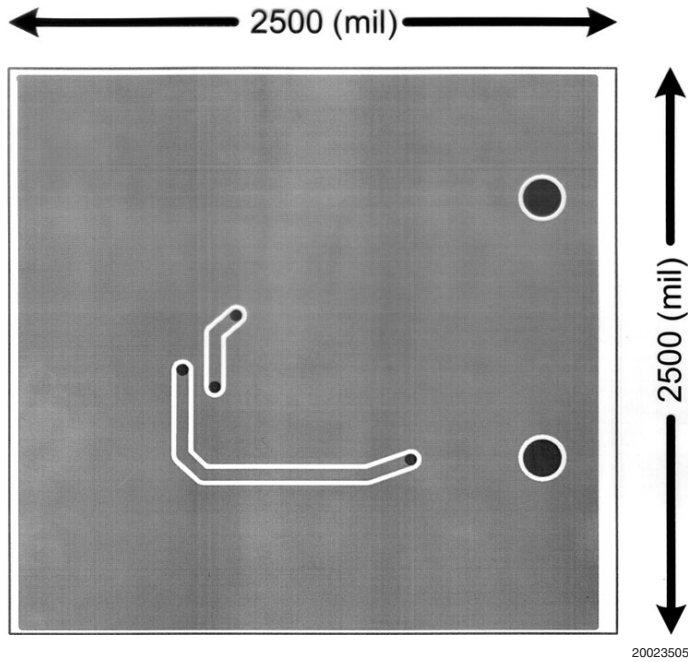


FIGURE 5. Back Side

## Notes

**LIFE SUPPORT POLICY**

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
Americas  
Email: support@nsc.com

www.national.com

**National Semiconductor Europe**

Fax: +49 (0) 180-530 85 86  
Email: europe.support@nsc.com  
Deutsch Tel: +49 (0) 69 9508 6208  
English Tel: +44 (0) 870 24 0 2171  
Français Tel: +33 (0) 1 41 91 8790

**National Semiconductor Asia Pacific Customer Response Group**

Tel: 65-2544466  
Fax: 65-2504466  
Email: ap.support@nsc.com

**National Semiconductor Japan Ltd.**

Tel: 81-3-5639-7560  
Fax: 81-3-5639-7507

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated